
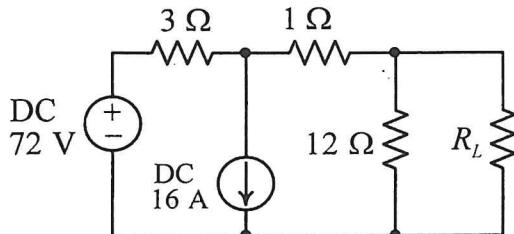


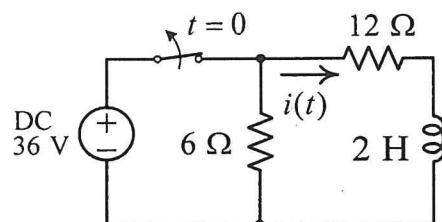

- 圖一之電路中，若電阻 R_L 欲獲得最大功率，試計算 R_L 之值及其所消耗之功率。(10%)
- 圖二電路中的開關已閉合很久，在 $t=0$ 時開啟，試計算 $t>0$ 時之電流 $i(t)$ 。(15%)




圖一




圖二

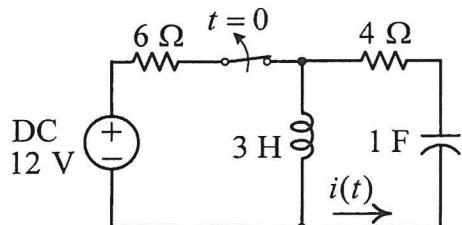- 圖三電路中的開關已閉合很久，在 $t=0$ 時開啟，試計算 $t>0$ 時之電流 $i(t)$ 。(25%)
- 請求出如圖四所示電路 $a-b$ 端之戴維寧等效電路，並繪出其等效電路圖。(15%)




圖三

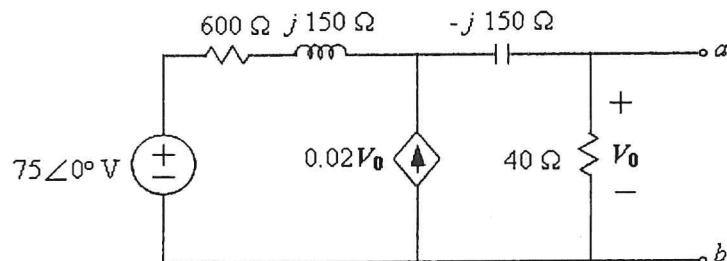


圖四

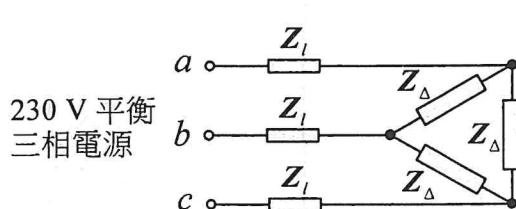- 某一平衡三相 Δ -接負載，其每相阻抗為 $Z_\Delta = 40 \angle 36.87^\circ \Omega$ ，經由線路阻抗為 $Z_l = 0.9+j1.2 \Omega$ 之導線連接於線電壓有效值為 230V 之平衡三相三線電源，如圖五所示，試回答以下問題：
 (a) 負載側之線電壓為多少？(10%)
 (b) 電源側所供應之三相複功率為何？(10%)
- 請計算如圖六所示網路之迴路電流 I_1 和 I_2 分別為多少？(15%)



圖五

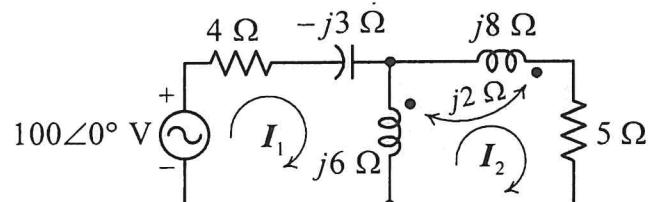

圖六



1. (15%) Solve the general solution of the following differential equations:
[解下列微分方程式之通解]
 - (1) $y' = 10e^{2x}$ (5 分); (2) $xy' + 2y = 2$ (5 分); (3) $\frac{dy}{dx} = 1 + e^{(y-x+1)}$ (5 分).
2. (10%) Solve $x^2y'' - xy' + y = 2x$ [求 Cauchy-Euler Equation 之通解].
3. (15%) Find the Laplace transform or inverse transform of the following functions:
 - (1) $f(t) = 4t^2 - e^{-3t} + 5 \sin 3t$; 求 $F(s) = L[f(t)]$ (5 分);
 - (2) $f(t) = t \int_0^t \sin t dt + \int_0^t \sin \tau \cos(t-\tau) d\tau$; 求 $F(s) = L[f(t)]$ (5 分);
 - (3) $F(s) = \frac{e^{-2s}}{s(s-1)(s+1)}$; 求 $f(t) = L^{-1}[F(s)]$ (5 分).
4. (10%) Use the Laplace transform to solve the given initial value problem [利用拉氏轉換求解以下微分方程式]: $\frac{dy(t)}{dt} - y(t) = te^t \sin t$, $y(0) = 0$.
5. (20%) Let A and B be $n \times n$ matrices. B is similar to A. Prove that the two matrices both have the same characteristic polynomial and consequently both have the same eigenvalues.
6. (20%) Solve the system

$$\begin{aligned}\dot{y}_1(t) &= 3y_1(t) + 4y_2(t) \\ \dot{y}_2(t) &= 3y_1(t) + 2y_2(t) \\ \text{with } y_1(0) &= 6, y_2(0) = 1\end{aligned}$$

$$\text{Find } Y = \begin{bmatrix} y_1(t) \\ y_2(t) \end{bmatrix}$$

7. (10%) Which of the following collections of vectors are linearly independent in R^3 ?

- (a) $[1,1,1]^T, [1,1,0]^T, [1,0,0]^T$
- (b) $[1,2,4]^T, [2,1,3]^T, [4,-1,1]^T$